

# Lab Report 8 – Design and Implementation of a Digital Up/Down Counter from 0 to 99

Arnav Yadnopavit – EE24BTECH11007

Prajwal – EE24BTECH11051

## 1 First digit

### BCD Up Counter State Transition Table (0 to 9 with Don't Cares)

Present State				Next State				T Inputs				Remark
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3^+$	$Q_2^+$	$Q_1^+$	$Q_0^+$	$T_3$	$T_2$	$T_1$	$T_0$	
0	0	0	0	0	0	0	1	0	0	0	1	0 → 1
0	0	0	1	0	0	1	0	0	0	1	1	1 → 2
0	0	1	0	0	0	1	1	0	0	0	1	2 → 3
0	0	1	1	0	1	0	0	0	1	1	1	3 → 4
0	1	0	0	0	1	0	1	0	0	0	1	4 → 5
0	1	0	1	0	1	1	0	0	0	1	1	5 → 6
0	1	1	0	0	1	1	1	0	0	0	1	6 → 7
0	1	1	1	1	0	0	0	1	1	1	1	7 → 8
1	0	0	0	1	0	0	1	0	0	0	1	8 → 9
1	0	0	1	0	0	0	0	1	0	0	1	9 → 0
1	0	1	0	X	X	X	X	X	X	X	X	Don't Care
1	0	1	1	X	X	X	X	X	X	X	X	Don't Care
1	1	0	0	X	X	X	X	X	X	X	X	Don't Care
1	1	0	1	X	X	X	X	X	X	X	X	Don't Care
1	1	1	0	X	X	X	X	X	X	X	X	Don't Care
1	1	1	1	X	X	X	X	X	X	X	X	Don't Care

### Karnaugh Maps for T Flip-Flop Inputs

Up Counter (Controlled by  $B_u \cdot \overline{B_d}$ )

$T_0$  (Up)

$$(T_0)_{up} = B_u \cdot \overline{B_d} \cdot 1 = B_u \cdot \overline{B_d}$$

	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$T_1$  (**Up**)

$$(T_1)_{up} = Q_0 \cdot \overline{Q_3} \cdot B_u \cdot \overline{B_d}$$

	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	X	X	X	X
10	0	0	X	X

$T_2$  (**Up**)

$$(T_2)_{up} = Q_0 \cdot Q_1 \cdot B_u \cdot \overline{B_d}$$

	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$T_3$  (**Up**)

$$(T_3)_{up} = Q_0 \cdot (Q_3 + Q_2 Q_1) \cdot B_u \cdot \overline{B_d}$$

	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	1	X	X

## BCD Down Counter State Transition Table (9 to 0 with Don't Cares)

Present State				Next State				T Inputs				Remark
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3^-$	$Q_2^-$	$Q_1^-$	$Q_0^-$	$T_3$	$T_2$	$T_1$	$T_0$	
1	0	0	1	1	0	0	0	0	0	0	1	9 → 8
1	0	0	0	0	1	1	1	1	1	1	1	8 → 7
0	1	1	1	0	1	1	0	0	0	0	1	7 → 6
0	1	1	0	0	1	0	1	0	0	1	1	6 → 5
0	1	0	1	0	1	0	0	0	0	0	1	5 → 4
0	1	0	0	0	0	1	1	0	1	1	1	4 → 3
0	0	1	1	0	0	1	0	0	0	0	1	3 → 2
0	0	1	0	0	0	0	1	0	0	1	1	2 → 1
0	0	0	1	0	0	0	0	0	0	0	1	1 → 0
0	0	0	0	1	0	0	1	1	0	0	1	0 → 9
1	0	1	0	X	X	X	X	X	X	X	X	Don't Care
1	0	1	1	X	X	X	X	X	X	X	X	Don't Care
1	1	0	0	X	X	X	X	X	X	X	X	Don't Care
1	1	0	1	X	X	X	X	X	X	X	X	Don't Care
1	1	1	0	X	X	X	X	X	X	X	X	Don't Care
1	1	1	1	X	X	X	X	X	X	X	X	Don't Care

**Down Counter (Controlled by  $\overline{B_u} \cdot B_d$ )**

$T_0$  (Down)

$$T_0 = \overline{B_u} \cdot B_d$$

	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$T_1$  (Down)

$$T_1 = \overline{Q_0} \cdot (Q_1 + Q_2 + Q_3) \cdot \overline{B_u} \cdot B_d$$

	00	01	11	10
00	0	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$T_2$  (Down)

$$T_2 = \overline{Q_1} \cdot \overline{Q_0} \cdot (Q_2 + Q_3) \cdot \overline{B_u} \cdot B_d$$

	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	X	X	X	X
10	1	0	X	X

$T_3$  (Down)

$$T_3 = \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \cdot \overline{B_u} \cdot B_d$$

	00	01	11	10
00	1	0	0	0
01	0	0	0	0
11	X	X	X	X
10	1	0	X	X

## Combined T Flip-Flop Expressions (Up and Down Modes)

$T_0$  (Overall)

$$T_0 = B_u \cdot \overline{B_d} + \overline{B_u} \cdot B_d$$

$T_1$  (Overall)

$$T_1 = Q_0 \cdot \overline{Q_3} \cdot B_u \cdot \overline{B_d} + \overline{Q_0} \cdot (Q_1 + Q_2 + Q_3) \cdot \overline{B_u} \cdot B_d$$

$T_2$  (Overall)

$$T_2 = Q_0 \cdot Q_1 \cdot B_u \cdot \overline{B_d} + \overline{Q_1} \cdot \overline{Q_0} \cdot (Q_2 + Q_3) \cdot \overline{B_u} \cdot B_d$$

$T_3$  (Overall)

$$T_3 = Q_0 \cdot (Q_3 + Q_2 Q_1) \cdot B_u \cdot \overline{B_d} + \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \cdot \overline{B_u} \cdot B_d$$

## 2 Second Digit

We know that the state transition table and k-maps for the second digit will be same but we have to ensure that second digit only changes when first digit either transits from 9 to 0 or 0 to 9 i.e

Present State				Next State				T Inputs				Remark
$Q_3$	$Q_2$	$Q_1$	$Q_0$	$Q_3$	$Q_2$	$Q_1$	$Q_0$	$T_3$	$T_2$	$T_1$	$T_0$	
0	0	0	0	1	0	0	1	1	0	0	1	$0 \rightarrow 9$
1	0	0	1	0	0	0	0	1	0	0	1	$9 \rightarrow 0$

Therefore,

$$\begin{aligned} T'_0 &= (T_0)_{up} \cdot \overline{Q_3} \cdot \overline{Q_0} + (T_0)_{down} \cdot \overline{Q_3} \cdot \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \\ T'_1 &= (T_1)_{up} \cdot \overline{Q_3} \cdot \overline{Q_0} + (T_1)_{down} \cdot \overline{Q_3} \cdot \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \\ T'_2 &= (T_2)_{up} \cdot \overline{Q_3} \cdot \overline{Q_0} + (T_2)_{down} \cdot \overline{Q_3} \cdot \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \\ T'_3 &= (T_3)_{up} \cdot \overline{Q_3} \cdot \overline{Q_0} + (T_3)_{down} \cdot \overline{Q_3} \cdot \overline{Q_2} \cdot \overline{Q_1} \cdot \overline{Q_0} \end{aligned}$$

## 3 Circuit Design

Mainly the circuit is built using logic gates and jk flip-flop

### 3.1 Components

- **Arduino Uno** – 1  
Provides 5V power and possibly input control (button pulse or clock).
- **Breadboards** – 3  
Two medium-sized for ICs and one large for extra wiring space.
- **74HC73 (JK Flip-Flop)** – 6  
Dual JK flip-flops with Clear; used for BCD counting and acts as T flip flop when J and K are shorted(4 bits per digit).
- **74HC00 (Quad 2-input NAND gate)** – 3  
Used for implementing logic conditions.

- **74HC08 (Quad 2-input AND gate)** – 3  
Used to enable logic outputs as per Karnaugh expressions.
- **74HC32 (Quad 2-input OR gate)** – 3  
Used to combine logic signals.
- **74HC04 (Hex Inverter / NOT gate)** – 2  
Used for inverting control and data signals.
- **CD4511 (BCD to 7-segment decoder)** – 2  
Drives 7-segment displays using 4-bit BCD input.
- **7-Segment Displays** – 2  
Likely common cathode; used to visually represent counter value.
- **Push Buttons** – 3  
Used for manual Up, Down, and Reset controls.
- **Resistors** – approximately 10–15  
Used for pull-down configurations and current limiting on LEDs.
- **Jumper Wires** – Multiple  
For all the required interconnections across components and breadboards.

### 3.2 Circuit Schematic



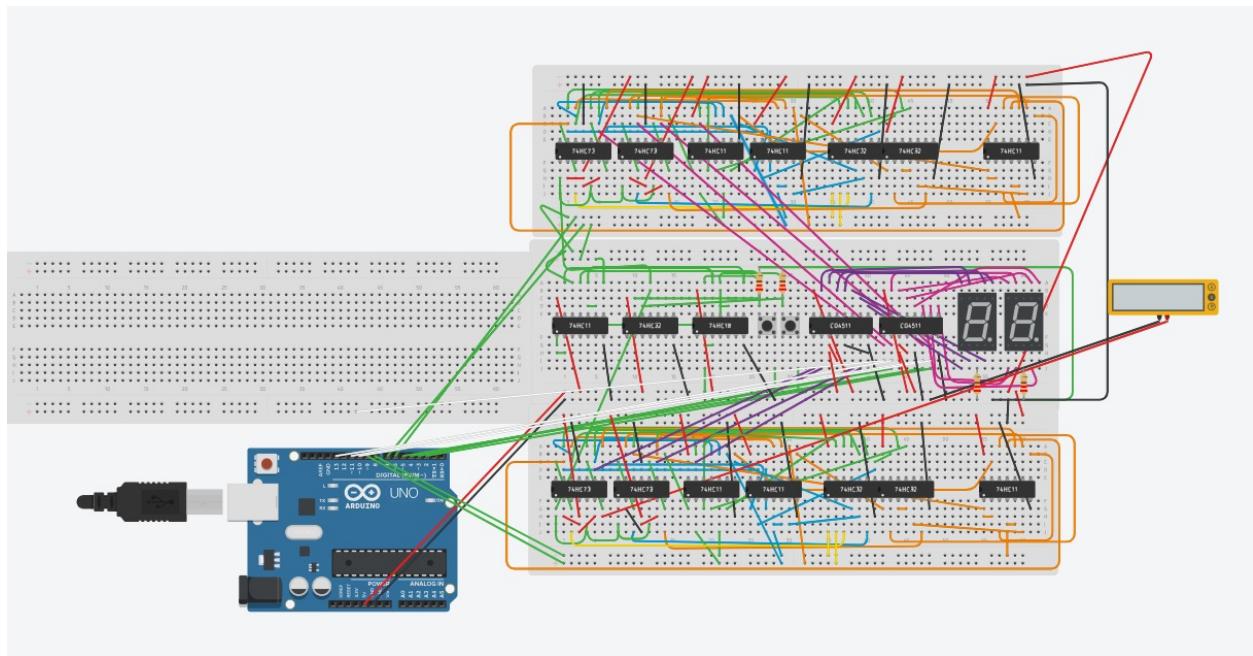



Figure 1: Breadboard implementation of a BCD up/down counter using T flip-flops and logic gates.


### 3.3 Wiring

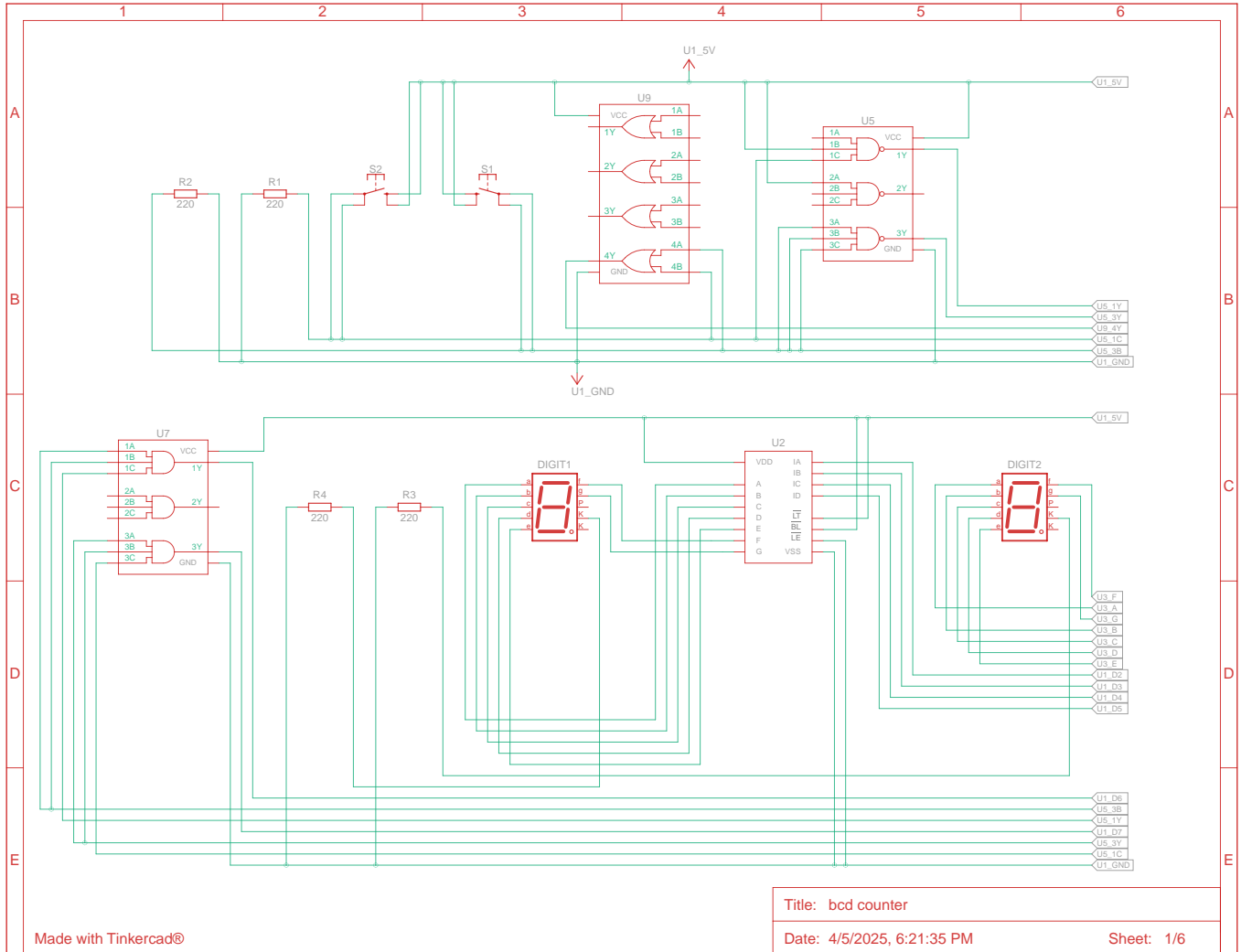


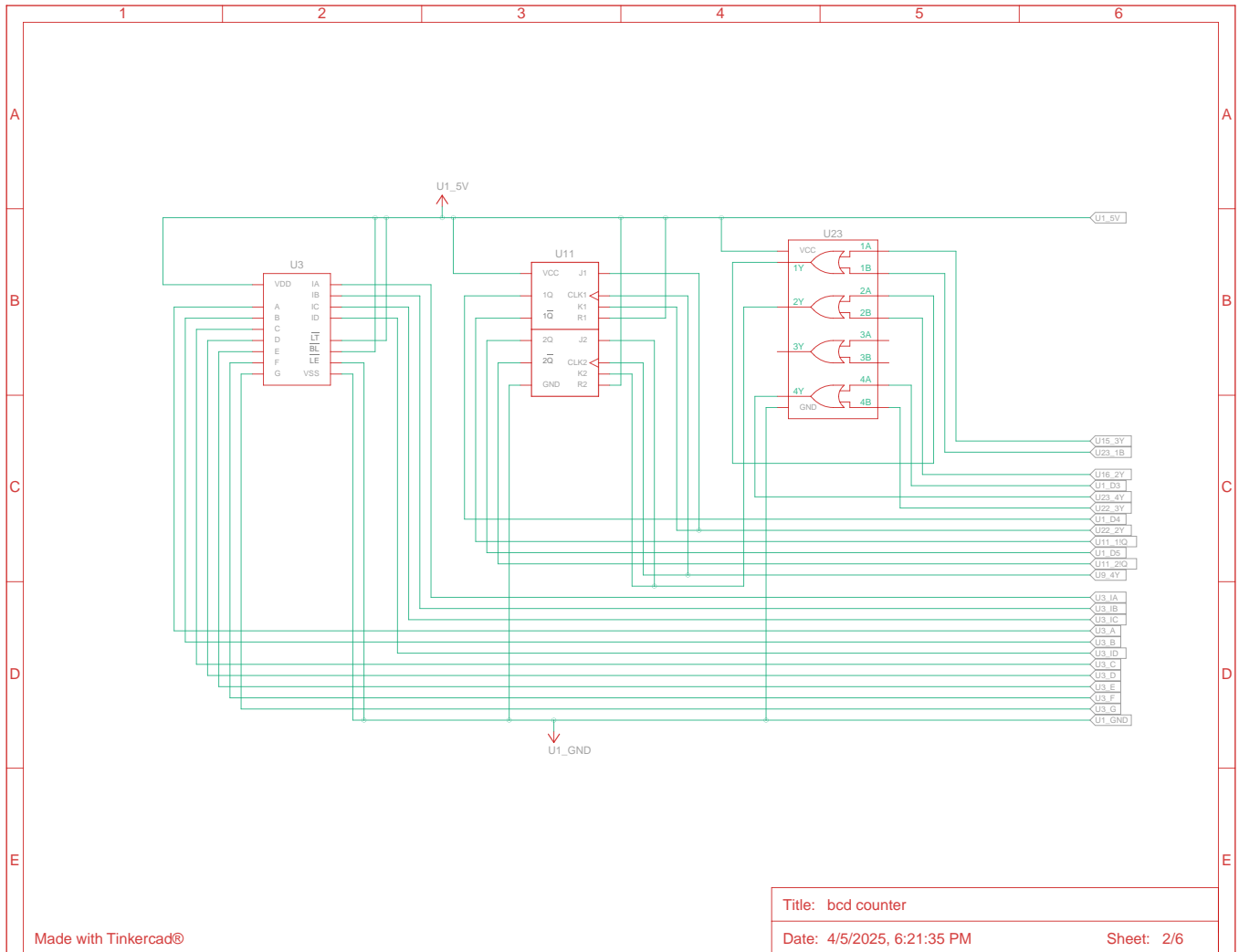




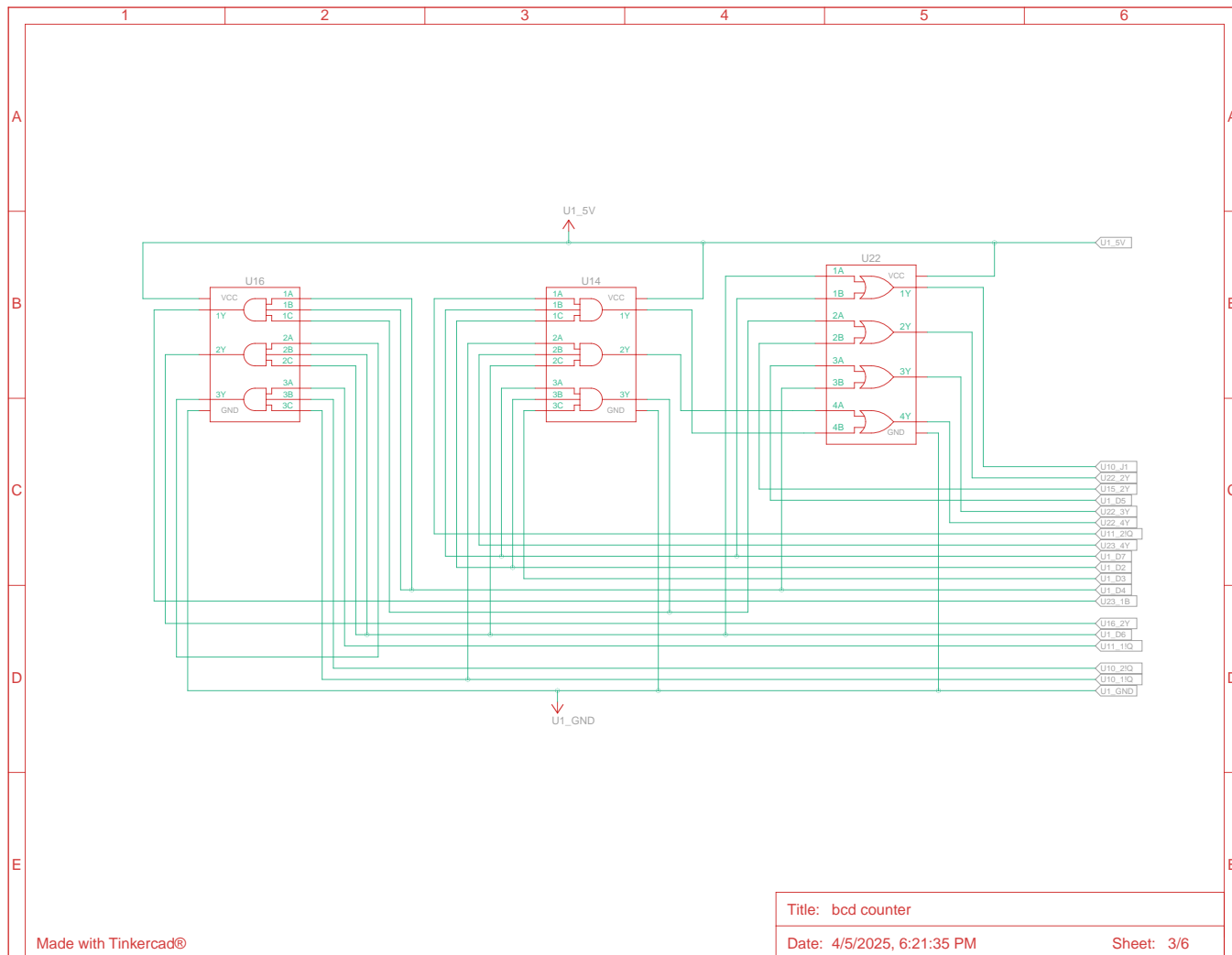

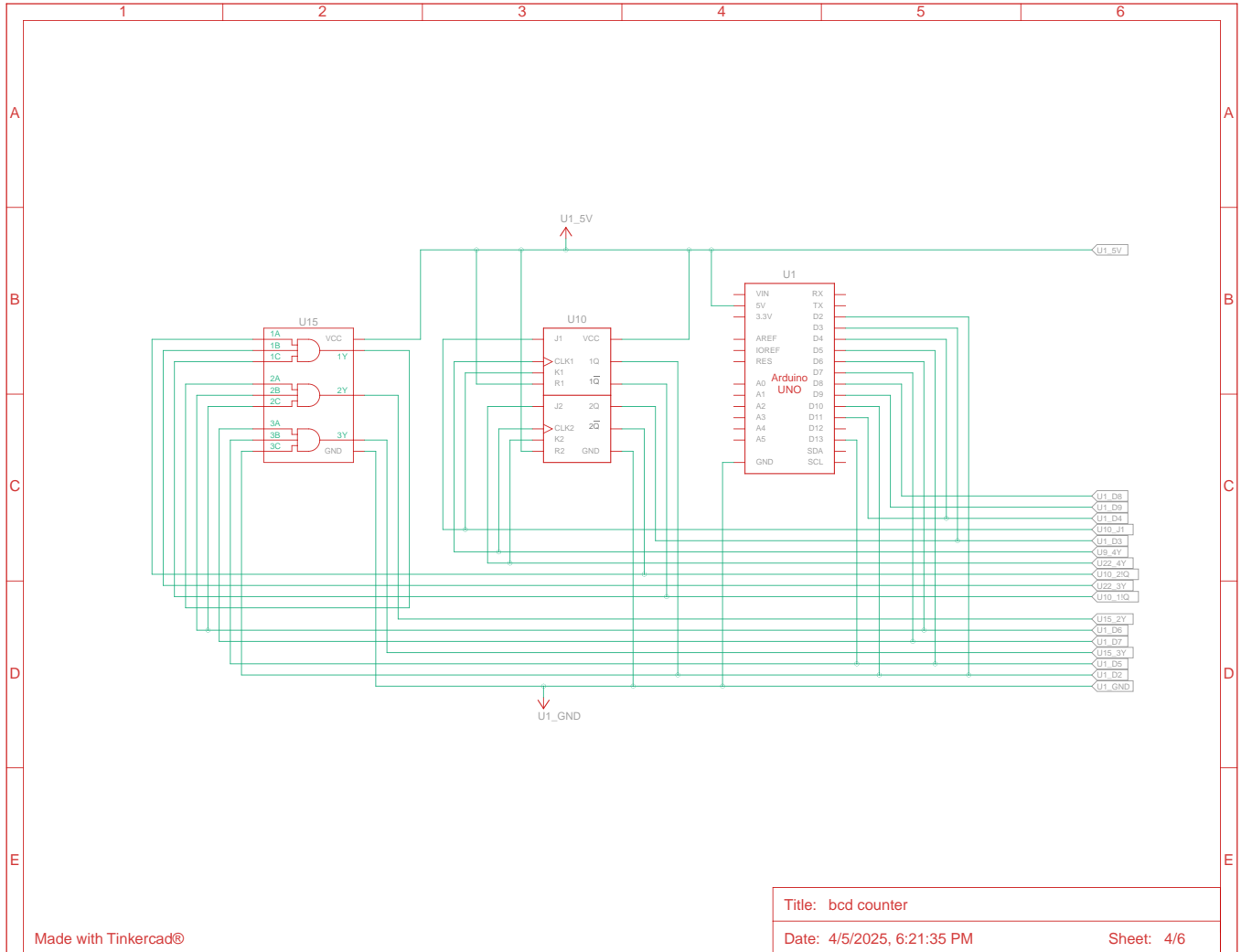

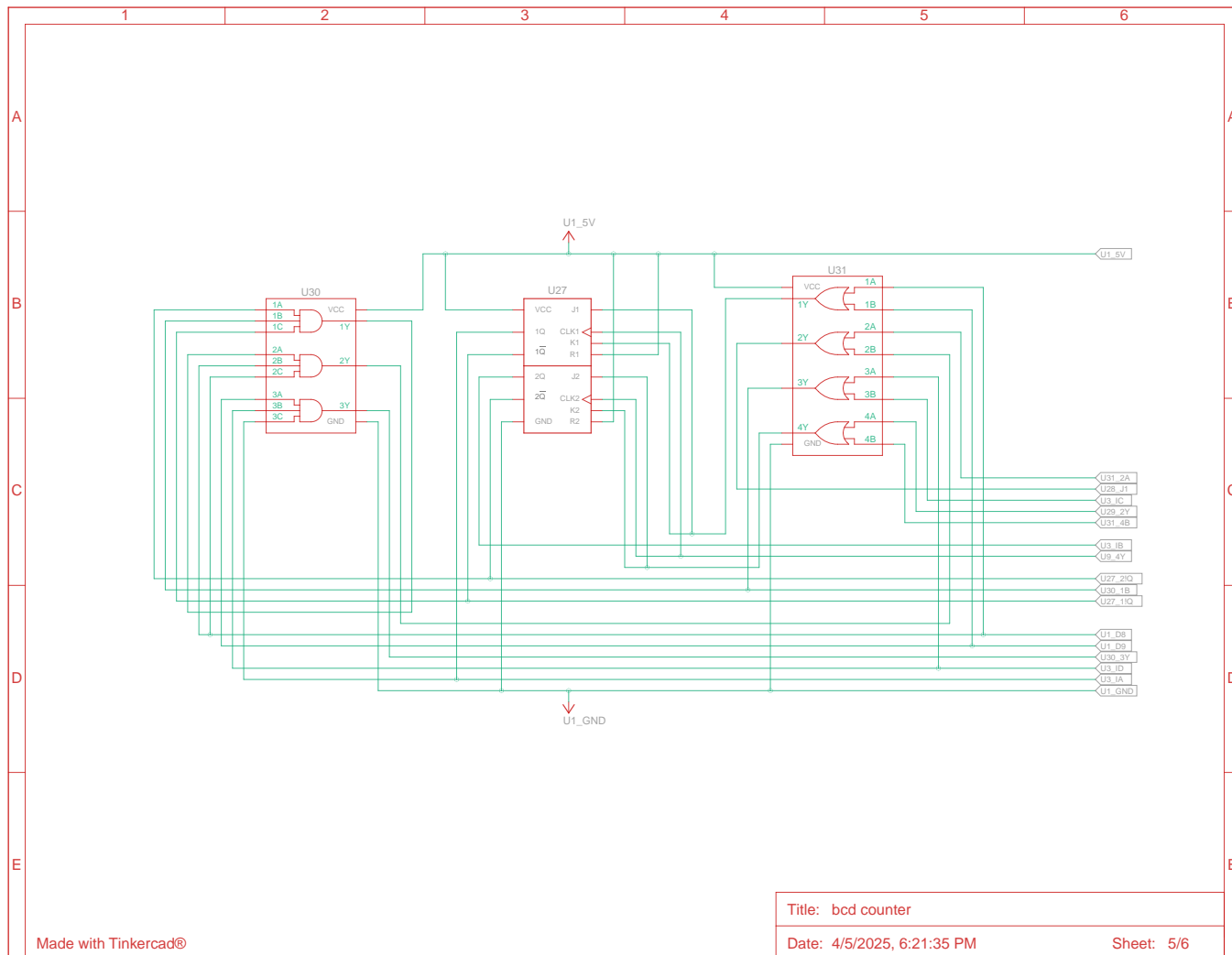

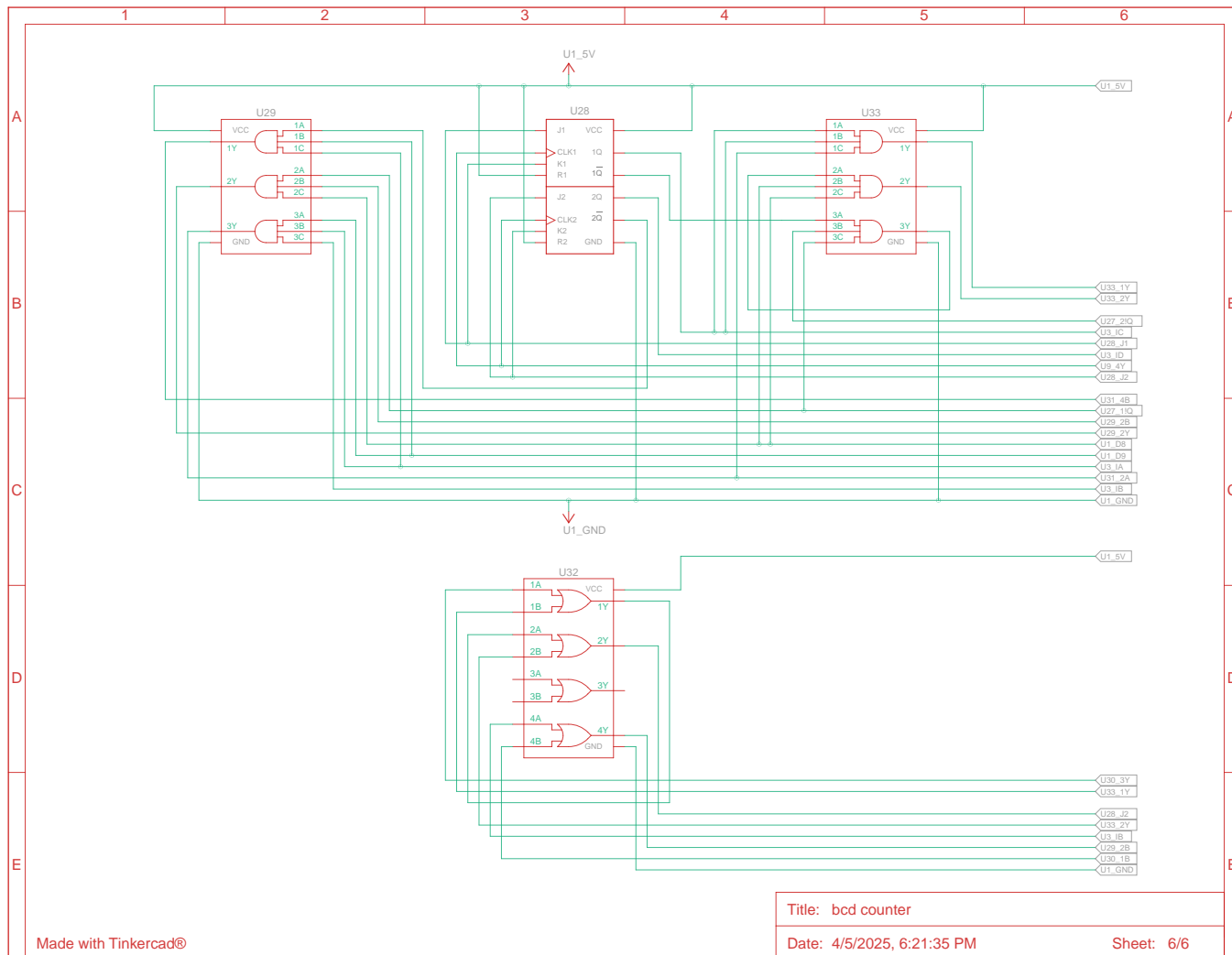

### **3.4 Simulation**

## **4 Conclusion**

The above circuit performs number counting from 0 to 99. When up button is pressed the number increases by one and down button is pressed number decreases by one