

LabReport9

Arnav Yadnopavit- EE24BTECH11007

Prajwal- EE24BTECH11051

April 19, 2025

Aim

To design and implement a Moore Finite State Machine (FSM) using T flip-flops to detect the overlapping sequence **11011**, and to analyze its state diagram, transition table, excitation equations, and output waveform.

Apparatus

- Logic simulator or breadboard setup
- Logic gates (AND, OR, NOT, XOR)
- T Flip-Flops (7476 ICs)
- Arduino
- LEDs for output
- Wires and connectors

Theory

Finite State Machines (FSM) are used to detect sequences. In a Moore machine, the output depends only on the present state.

Sequence to Detect: 11011 (Overlapping allowed)

States and Transitions

- S0: Initial state
- S1: Received '1'
- S2: Received '11'

- S3: Received '110'
- S4: Received '1101'
- S5: Sequence '11011' detected

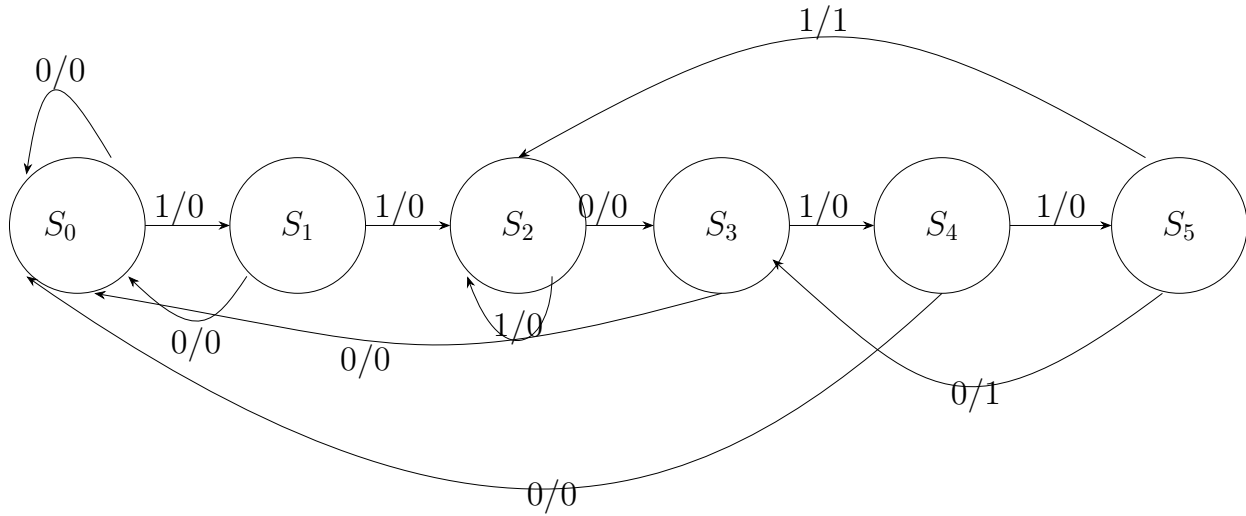


Figure 1: State Diagram

State Encoding

State	Encoding (Q2 Q1 Q0)
S0	000
S1	001
S2	010
S3	011
S4	100
S5	101

Output

- Output = 1 only in state S5
- Output = 0 in all other states

Finding Minterms

Q_2	Q_1	Q_0	x	T_2	T_1	T_0	Q_{2next}	Q_{1next}	Q_{0next}	y
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	1	0
0	0	1	0	0	0	1	0	0	0	0
0	0	1	1	0	1	1	0	1	0	0
0	1	0	0	0	0	1	0	1	1	0
0	1	0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	1	0	0	0	0
0	1	1	1	1	1	1	1	0	0	0
1	0	0	0	1	0	0	0	0	0	0
1	0	0	1	0	0	1	1	0	1	0
1	0	1	0	1	1	0	0	1	1	1
1	0	1	1	1	1	1	0	1	0	1
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

		Q_0x			
		00	01	11	10
Q_2Q_1	00	0	0	0	0
	01	0	0	1	0
	11	X	X	X	X
	10	1	0	1	1

T_2

		Q_0x			
		00	01	11	10
Q_2Q_1	00	0	0	1	0
	01	0	0	1	1
	11	X	X	X	X
	10	0	0	1	1

		T_1			
		Q_0x			
		00	01	11	10
Q_2Q_1	00	0	1	1	1
	01	1	0	1	1
	11	X	X	X	X
	10	0	1	1	0

T_0

Expressions are as follows



$$T_2 = Q_1Q_0x + Q_2Q_1'Q_0 + Q_2Q_1'x'$$

$$T_1 = Q_0x + Q_2'Q_1Q_0 + Q_2Q_1'Q_0$$

$$T_0 = Q_1'x + Q_1x' + Q_0Q_2'$$

$$y = Q_2Q_1'Q_0$$

Observations

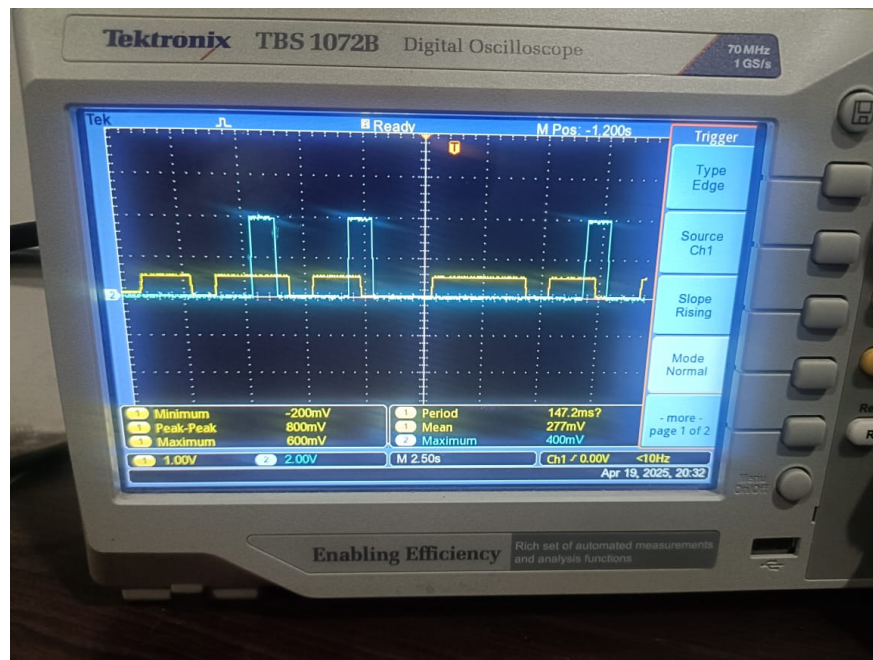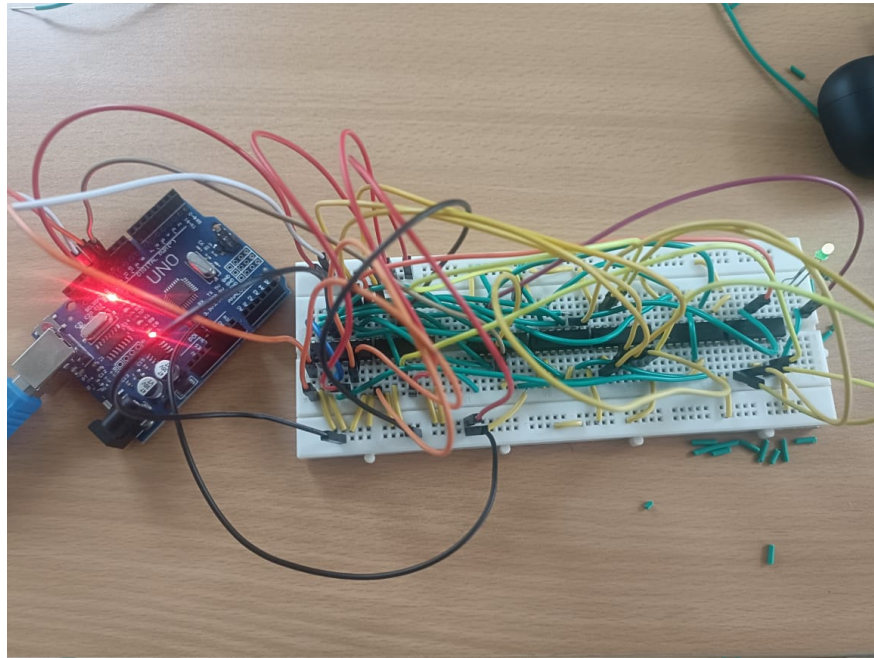

Result

The FSM successfully detects the sequence **11011** and produces an output '1' whenever the sequence is detected, including overlapping instances.

To refer arduino code and working video refer to

<https://github.com/ArnavYadnopavit/ElectricalLabEE1200/tree/main/LabReport9>
Thank you